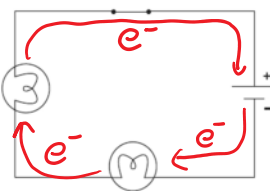
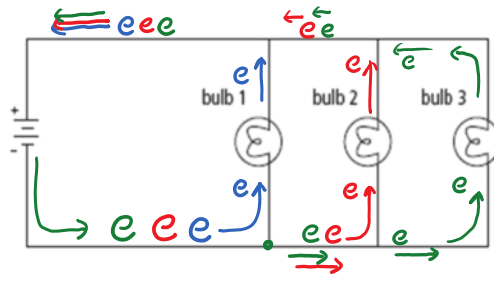
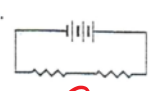



Science 9 – 3-4 C2: Series vs. Parallel Circuit Part 1


In a circuit, devices (such as light bulbs or batteries) can be placed in two different ways.


SERIES	PARALLEL
<ul style="list-style-type: none"> <li>When devices are placed in series, the current must go through <u>each devices</u> one by one</li> <li>In this circuit, there is only <u>one path</u> and the <u>electrons</u> goes through the two light bulbs in the series.</li> </ul> 	<ul style="list-style-type: none"> <li>When devices are placed in parallel, there are <u>2 or more pathways</u> for the electron current to travel</li> <li>it <u>splitt</u> and some of it goes through one device, and some of it goes through the other(s).</li> </ul> 


Decide whether each circuit is Series, Parallel, or a Combination of the two.


A.  S

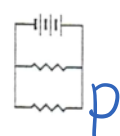B.  P

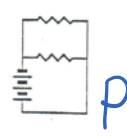C.  P

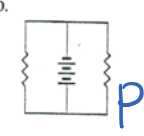
D.  P

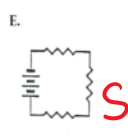E.  S

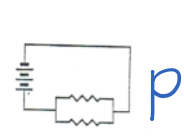F.  P

Series and Parallel Combinations of Cells


- When cells are connected in Series, we can find the total amount of voltage by just add them together.

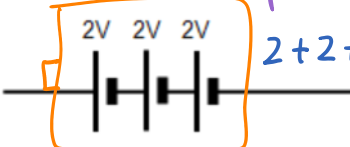  $2 + 2 + 2 = 6V$

*power!!!*

*In Series*  
 $V_T = V_1 + V_2 + V_3 + \dots$

- When cells are combined in parallel, the voltage will not increase but the amount of charge (current) does.

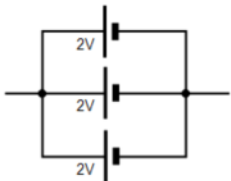
  $V_{Total} = 2V$


*but it will last ~3 times longer*

- The advantage of the parallel circuit is that although the output voltage is the same as that of a single cell, the battery formed from the group of cells contains more energy and so will supply current for longer.

- Voltage is measured by a device called a Voltmeter



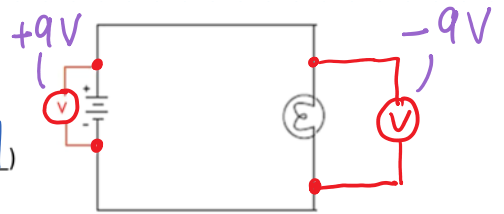- Voltage is measured by a device called a Voltmeter
- The symbol for the device is  on a circuit diagram
- The voltmeter is always connected across the device in (parallel)
- This is to measure the Voltage (Energy) difference between 2 points




### Measuring Voltage in Series

- When electrons go through a cell they gain Energy, we call this Voltage Gain
- AS electrons go through a load such as a light bulb they lose Energy, we call this Voltage Drop
- In an ideal situation the total voltage gained from the battery should Equal to the total voltage dropped from all the loads combined.

$$V_{Total} = V_1 + V_2 + V_3 + \dots$$

Series

HW: WB P. 140

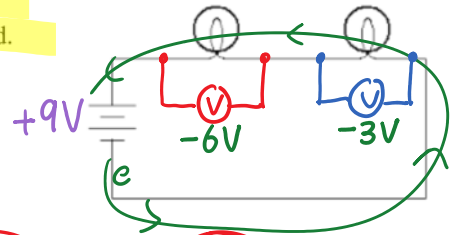


Example 1)

What is  $V_T$ ?

$$\text{Total Voltage} = 10V + 35V + 45V + 20V$$


$$V_T = 110V$$

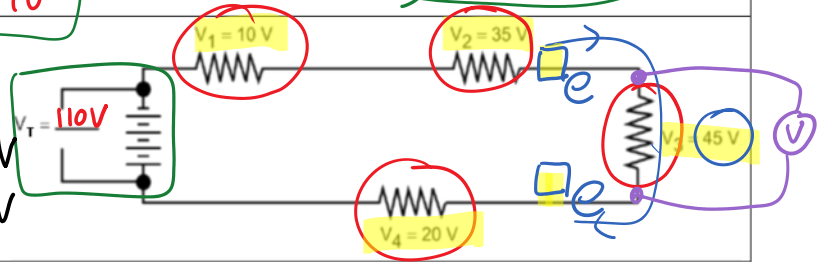

### Measuring Voltage in Parallel

- When electrons go through devices in parallel they split at the junction point.
- Each load in parallel will receive the Same amount of energy/Voltage.

$$V_{Total} = V_1 = V_2 = V_3 \dots$$

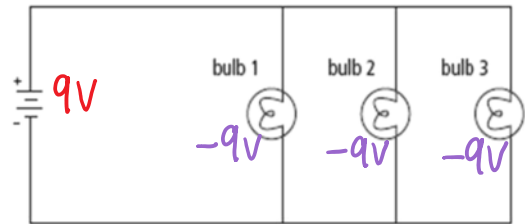

Example)

If  $V_1 = 10V$ , Calculate  $V_T$ ,  $V_2$  and  $V_3$

