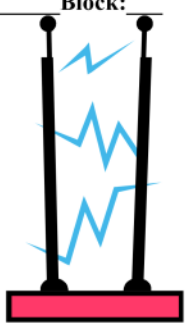





Calculating Voltage in Series



Circle the best term in the parentheses to correctly complete each statement.

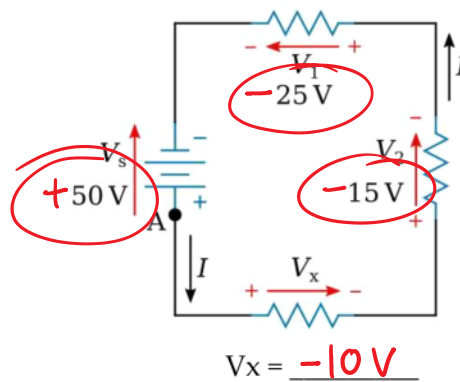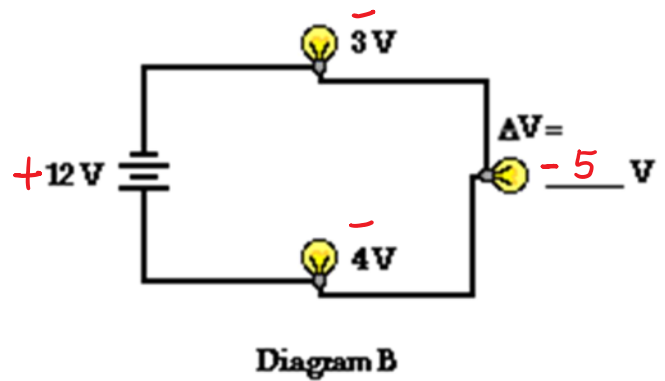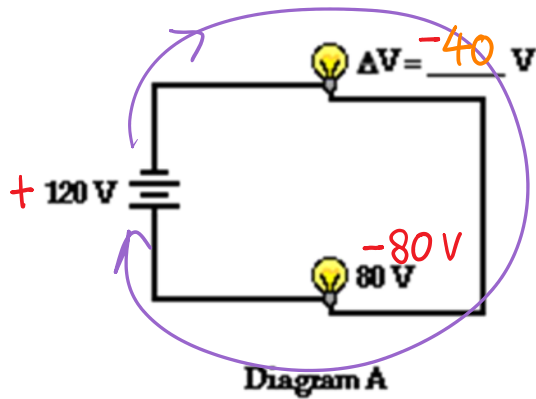- 1) A series circuit has (*more than one*, only one) path for current to travel.
- 2) If two different resistors are connected in series, the voltage across one resistor will be (*equal to*, different from) the voltage across the second resistor.
3. The sum of the Energy voltages across each of the resistors in a series circuit is (equal to, *different from*) the total voltage supplied by the battery.

Find the unknown voltage at V in each of the following circuits.



Calculating Voltage in Parallel




Circle the best term in the parentheses to correctly complete each statement.

1. A parallel circuit has (*only one*, more than one) path for current to travel.

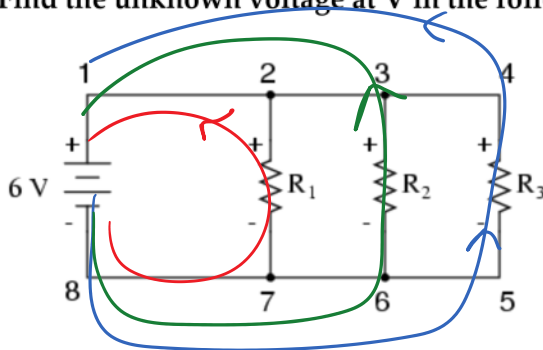2. If two different resistors are connected in parallel, the voltage across one resistor will be (*equal to*, different from) the voltage across the second resistor.

Find the unknown voltage at V in the following circuits.



$$V_1 = \underline{6V}$$


$$V_2 = \underline{6V}$$

$$V_3 = \underline{6V}$$


Calculating Voltage in Mixed Circuit




Example

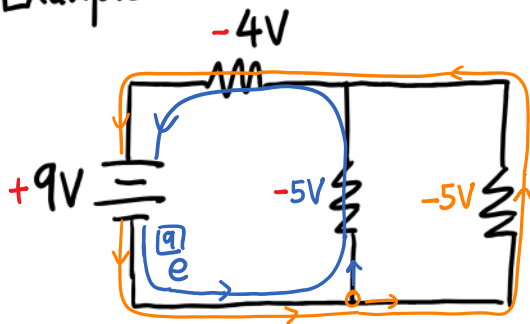

Q1,

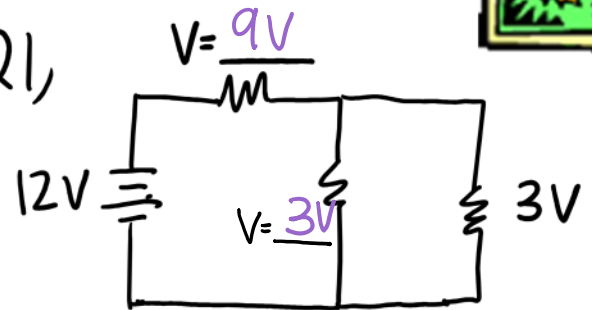

Q2)

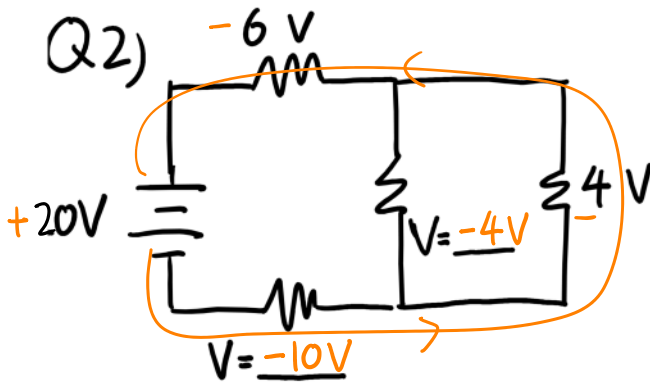

Q3)

