

PHYSICS 11


Circuits

Practice Test

Name: Key

Written Answer Questions

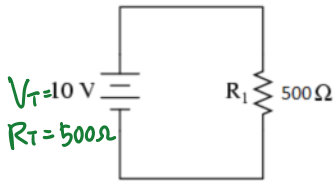- 1) Consider the simple circuit. [6 pts total]
 a) Determine the current in R1. [2 marks]



$$V_T = I_T R_T$$

$$10 = I_T (500)$$

$$I_T = 0.02 A$$

I_T too

1a) 0.02 A

- b) Determine the power draw for R1. [2 marks]

$$P_i = I_i^2 R_i = (0.02)^2 \cdot 500 = 0.2 \text{ Watt.}$$

1b) 0.2 W


- c) Determine the energy used by R1 if it is connected to the circuit for 10 minutes. [2 marks]

$$P = \frac{E}{t} \quad E = P \cdot t = 0.2 \text{ W} (600 \text{ sec}) = 120 \text{ J}$$

1c) 120 J

- 2) Determine the equivalent resistance for the following resistor networks. Use the following resistances:
 R1 = 20 Ω R2 = 80 Ω R3 = 100 Ω R4 = 200 Ω


a) [2 marks]

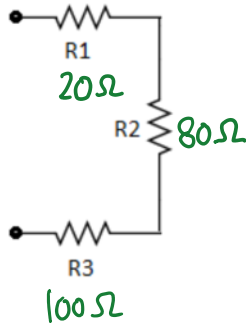

$$R_T = 20 + 80 + 100$$

$$R_T = 200 \Omega$$

b) [3 marks]

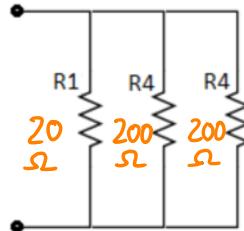


$$\frac{1}{R_T} = \frac{1}{20} + \frac{1}{200} + \frac{1}{200}$$

$$\frac{1}{R_T} = 0.06$$

$$R_T = \frac{1}{0.06} = 16.7 \Omega$$

c) [3 marks]

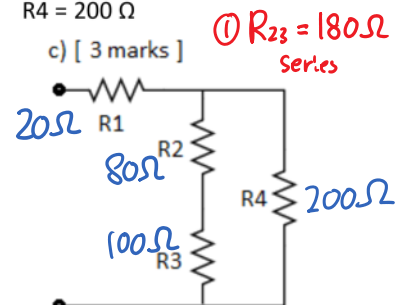

① R₂₃ = 180 Ω
Series

$$\textcircled{2} \frac{1}{R_{234}} = \frac{1}{180} + \frac{1}{200} \quad R_{234} = 94.7 \Omega$$

$$\textcircled{3} R_T = R_{234} + R_1 = 114.7 \Omega$$

2a) 200 Ω

2b) 16.7 Ω

2c) 114.7 Ω

① $R_{34} = 17\Omega$

$\frac{1}{R_{234}} = \frac{1}{10} + \frac{1}{17}$ $R_{234} = 6.3\Omega$

3) Consider the circuit pictured to the right. Determine the following:

a) The current through the 7.0Ω resistor [4 marks]

③ $V_T = I_T R_T$
 $6 = I_T \cdot 11.3$
 $I_T = 0.531A$

④ $V_1 = I_1 R_1$
 $V_1 = 0.531(5)$
 $V_1 = 2.656V$

⑤ $I_2 = \frac{V_2}{R_2}$
 $I_2 = \frac{3.34}{10}$
 $I_2 = 0.334A$

② $R_T = 5 + 6.3$
 $R_T = 11.3\Omega$


$(I_T) I_1 = 0.531A$

$V_1 = 2.656V$

$R_1 = 5.0\Omega$

$I_T = 0.531A$

$V_T = 6.0V$
 $R_T = 11.3\Omega$

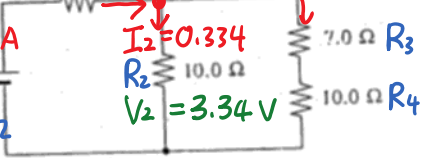

⑥ Junction

$I_T = I_2 + I_3$

$0.531 = 0.334 + I_3$

$I_3 = \dots$

3a) $0.197A$


b) The charge (Q is measured in Coulomb) that passes through the 7.0Ω resistor in 20.0 seconds [2 marks]

$0.197 \rightarrow I = \frac{Q}{t}$ $t = 20\text{sec}$

3b) $3.88C$

4) Consider the circuit to the right. Note that resistor $r = 4.0\Omega$ is internal resistance.

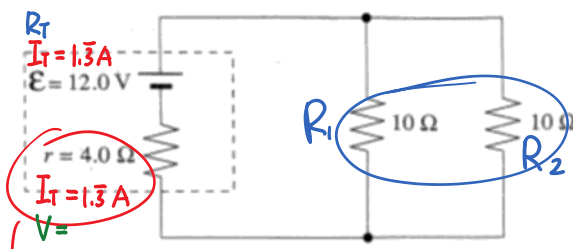a) Determine the terminal voltage. (Hint: you will need I_T first) [4 marks]



$\frac{1}{R_{12}} = \frac{1}{10} + \frac{1}{10}$ $R_{12} = 5\Omega$

$R_T = 5\Omega + 4\Omega = 9\Omega$

$V_T = I_T R_T$

$12V = I_T (9)$

$I_T = 1.3A$

4a) $6.67V$


$V_{\text{term}} = \mathcal{E} - I_T \cdot r = 12 - 1.3 \cdot (4) = 6.67V$

b) What is the total power consumed by the circuit that is lost to the internal resistance? [2 marks]

$P = I^2 \cdot r = (1.3)^2 \cdot (4\Omega) = 7.1\text{Watt}$

4b) 7.1Watt

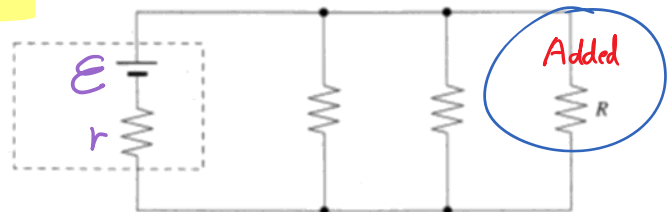c) Another resistor R is added to the circuit from Question 4, giving the circuit shown to the right. Does this increase, decrease or have no effect on terminal voltage? Justify your answer. [2 marks]



path
Add R in parallel \rightarrow Reduce traffic
 $R_T \downarrow$ (dec)

$\mathcal{E} = I_T R_T \rightarrow I_T \uparrow$ (inc)

$V_{\text{terminal}} = \mathcal{E} - I_T \cdot r$

$\therefore V_{\text{terminal}} \text{ dec !!}$
4c)

Current Split method for Q3

